

# LIC ESE MAY 2021 OBJECTIVE

Your email will be recorded when you submit this form

Not [singhsparsh@kccemsr.edu.in](mailto:singhsparsh@kccemsr.edu.in)? [Switch account](#)

\* Required

## Objective Questions

\*

For a Wein Bridge oscillator, the RC networks in the feedback circuit have values of their resistances  $R = 3.3 \text{ k}\Omega$  and capacitances  $C = 0.047 \text{ }\mu\text{F}$ ,

- ☒ Its frequency of oscillation is  $\approx 1 \text{ kHz}$
- ☐ Its frequency of oscillation is  $\approx 3.030 \text{ kHz}$
- ☐ Its frequency of oscillation is  $\approx 3.3 \text{ kHz}$
- ☐ Its frequency of oscillation is  $\approx 480 \text{ Hz}$

\*

For a Phase Locked Loop which of the following is true?

- ☒ Lock in range  $>$  Capture range
- ☐ Lock in range  $<$  Capture range
- ☐ Lock in range  $=$  Capture range
- ☐ Lock in range  $=$  half of Capture range



A square waveform having ON time greater than its OFF time is fed as input to an integrator. The resulting output of the integrator is called

- ☒ Triangular waveform
- ☐ Sawtooth waveform
- ☐ Inverted Square waveform
- ☐ Sine waveform

Clear selection

\*

For High voltage, High current voltage regulator using IC 723, output voltage and output currents respectively have one of the following correct values.

- ☐ Less than 7 V, greater than 150 mA
- ☒ Less than 7 V, less than 150 mA
- ☐ 7 to 37 V, greater than 150 mA
- ☐ 7 to 37 V, less than 150 mA

An ideal op-amp requires infinite bandwidth because

- ☒ Signals can be amplified without attenuation
- ☐ Output common-mode noise voltage is zero
- ☐ Output voltage occurs simultaneously with input voltage changes
- ☐ Output can drive infinite number of devices

Clear selection



An Inverting Schmitt trigger employs

- ☐ Only Negative feedback
- ☒ Only Positive feedback
- ☐ Both Negative and Positive feedback
- ☐ No feedback

Clear selection

A current to voltage converter converts

- ☒ Input current to proportional output voltage.
- ☐ Input current to proportional output current.
- ☐ Input voltage to proportional output voltage.
- ☐ Input voltage to proportional output current.

Clear selection

\*

The reference voltage of upper comparator used in functional block diagram of IC 555 is

- ☐  $1/5 V_{CC}$
- ☐  $1/3 V_{CC}$
- ☒  $2/3 V_{CC}$
- ☐  $2/5 V_{CC}$




\*

An integrator circuit

- ☐ uses a resistor in its feedback circuit.
- ☐ uses an inductor in its feedback circuit.
- ☒ uses a capacitor in its feedback circuit.
- ☐ uses a diode in its feedback circuit.

\*

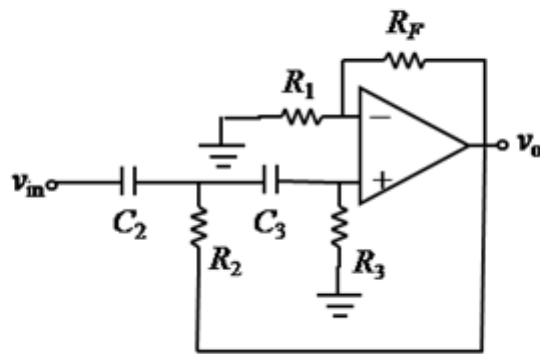The filter shown below has  $R_1 = 27 \text{ k}\Omega$ ,  $R_F = 15.8 \text{ k}\Omega$ ,  $R_2 = R_3 = 33 \text{ k}\Omega$ ,  $C_2 = C_3 = 0.0047 \text{ }\mu\text{F}$  is a



- ☒ High Pass filter with cut off frequency  $\approx 1 \text{ kHz}$
- ☐ High Pass filter with cut off frequency  $\approx 10 \text{ kHz}$
- ☐ Low Pass filter with cut off frequency  $\approx 1 \text{ kHz}$
- ☐ Low Pass filter with cut off frequency  $\approx 10 \text{ kHz}$



The output pulse width of a monostable multivibrator using 555 where R and C are the external components is

- ☐ RC
- ☒  $1.1 RC$
- ☐  $(2/3) RC$
- ☐  $(1/3) RC$

Clear selection

\*

In an Astable multivibrator if  $R_A=25K\Omega$ ,  $R_B=33k\Omega$ ,  $C=0.5\mu F$ , calculate discharging time of capacitor waveform

- ☒ 11.43 ms
- ☐ 20 ms
- ☐ 12.5 ms
- ☐ 10 ms

\*

Which of these circuits clips one half cycle of a sinusoidal waveform?

- ☐ Comparator
- ☐ Schmitt Trigger
- ☒ Half Wave Precision Rectifier
- ☐ Peak detector



In an inverting amplifier using op-amp

- ☐ The input is connected to the non-inverting terminal via resistor and inverting terminal is kept floating
- ☐ The input is connected to the non-inverting terminal via resistor and inverting terminal is grounded
- ☐ The input is connected to the inverting terminal via resistor and non- inverting terminal is kept floating
- ☒ The input is connected to the inverting terminal via resistor and non- inverting terminal is grounded

[Clear selection](#)For a non inverting comparator, input signal and reference voltage are given to

- ☐ inverting terminal of the op-amp through separate resistors
- ☐ non-inverting terminal of the op-amp through separate resistors
- ☐ inverting terminal and non-inverting terminal of the op-amp respectively
- ☒ non-inverting terminal and inverting terminal of the op-amp respectively

[Clear selection](#)

\*

| Output voltage of LM317 can be adjusted from

- ☐ -1.2 V to 37 V
- ☐ -1.2 V to -37 V
- ☒ 1.2 V to 37 V
- ☐ 1.2 V to -37 V




\*

In IC7805 the output voltage is

- ☒ 5 V
- ☐ 0 V
- ☐ 8 V
- ☐ 7 V

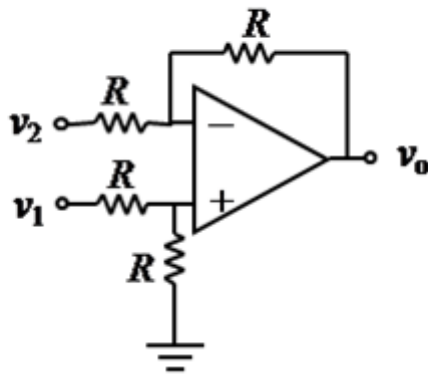**For the difference amplifier shown below, the output voltage is given by**



- ☐  $v_o = v_1 + v_2$
- ☐  $v_o = v_1 - v_2$
- ☒  $v_o = -v_1 + v_2$
- ☐  $v_o = -(v_1 + v_2)$

Clear selection




\*

Which one of these ICs is a Voltage Controlled Oscillator?

- ☐ IC 565
- ☒ IC 566
- ☐ IC 555
- ☐ IC 723

\*

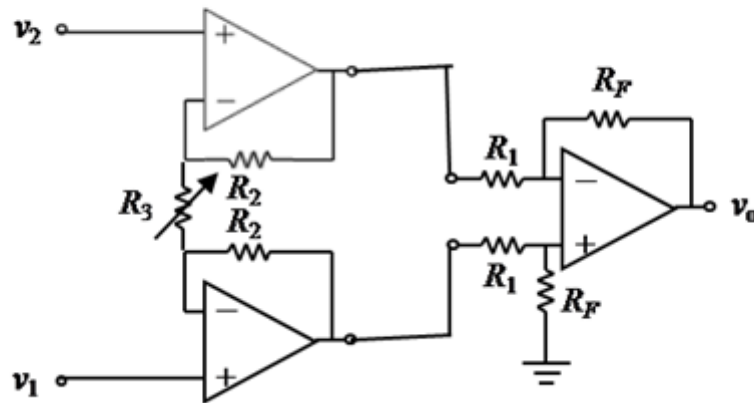The instrumentation amplifier shown in diagram has  $R_1 = R_F = 25 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ , and  $R_3$  varying from  $100 \Omega$  to  $1 \text{ k}\Omega$ , the voltage gain of the amplifier varies from



- ☐ 10 to 100
- ☒ 21 to 201
- ☐ 1 to 101
- ☐ 2 to 202

Page 2 of 2

[Back](#)[Submit](#)

Never submit passwords through Google Forms.

This form was created inside of K.C.College of Engineering And Management Studies And Research. [Report Abuse](#)



Google Forms



